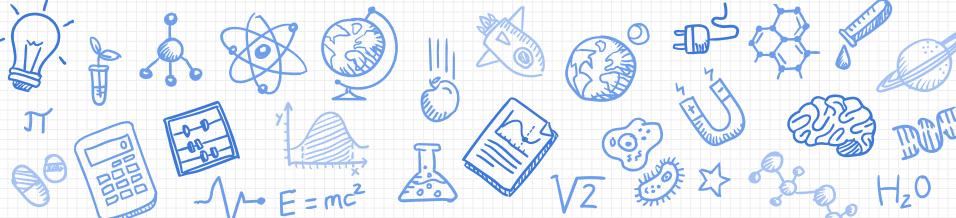
# EE16A Imaging 1

You must use a lab station computer!
Waitlisted / EECS47D wait by round table



#### **IMPORTANT: WAITLIST POLICY**

If lab is full, we will kick out **all** waitlisted folks

If full: We will check CalCentral enrollment after the presentation



#### Why?

#### Imaging 1:

- Finding a link between physical quantities and voltage is powerful
- If you can digitize it, you can do anything (IOT devices, internet, code, processing)




#### Today's Lab: Imaging Part 1

- ✗ Distribute materials (TI MSP430F5529)
  - X Bring your kit every week
- Breadboarding 101
- ✗ Build circuit that reacts to light intensity
  - Use Oscilloscope and MSP430 to see how the circuit behaves
- ✗ Graded checkoff starts today!



# **Light-detecting Circuit**

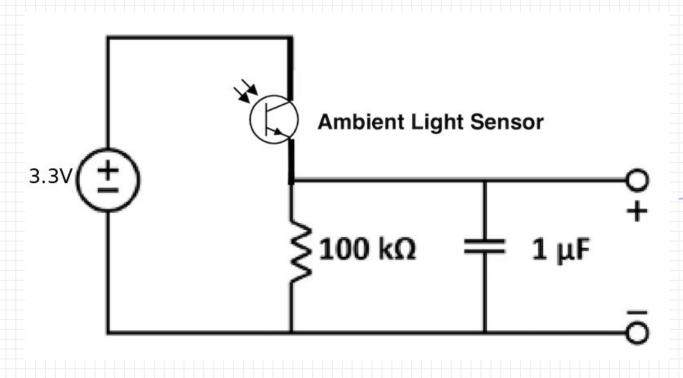




- **X** Components
  - X Resistors
  - Capacitors
  - X Voltage Source
- Wires / Jumpers [male-to-male vs male-to-female]



# What's in your bag?: Resistors

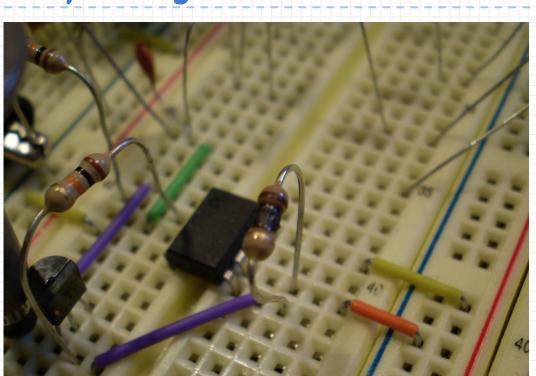






# What's in your bag?: Resistors

	4 Band Res	sistor Color Co	oding	
COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	<b>x1</b> Ω	
BROWN	1	1	x10Ω	±1%
RED	2	2	x100Ω	±2%
ORANGE	3	3	x1000Ω	
YELLOW	4	4	x10000Ω	
GREEN	5	5	x100000Ω	±0.5%
BLUE	6	6	x1000000Ω	±0.25
VIOLET	7	7	x10000000Ω	±0.10
GREY	8	8		±0.05
WHITE	9	9		
GOLD			0.1	±5%
SILVER			0.01	±10%




# **Equipment for Today: Capacitors**

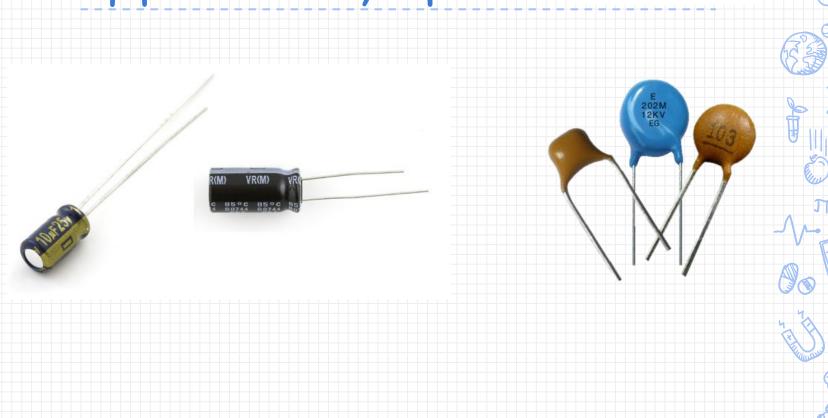



# **Equipment for Today: Wires/Jumpers**
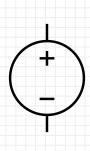
# Equipment for Today: Voltage Source (0.1 A Limit)










- **X** Components
- × Nodes
  - × Point in circuit where circuit elements meet
  - Wire between components are considered part of one node
- ★ We know you don't know much about circuits yet; we've given you very detailed instructions on how to build the circuit in the lab



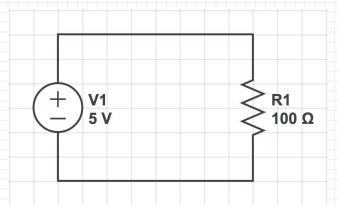
- Components (Resistors, LEDs, Capacitors)
- Nodes
  - Point in circuit where circuit elements meet
  - Wire between components are considered part of one node



What components?
How many nodes?
Where are these nodes?



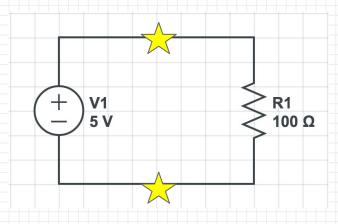- Components (Resistors, LEDs, Capacitors)
- Nodes
  - × Point in circuit where circuit elements meet
  - Wire between components are considered part of one node




What components?

Resistor, Voltage source

How many nodes? 2

Where are these nodes?

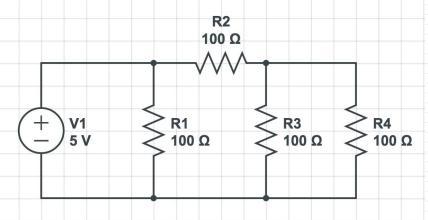- Components (Resistors, LEDs, Capacitors)
- Nodes
  - Point in circuit where circuit elements meet
  - × Wire between components are considered part of one node




What components?

How many nodes?

Where are these nodes?



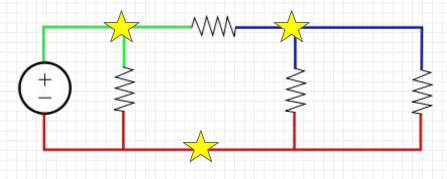- Components (Resistors, LEDs, Capacitors)
- × Nodes
  - Point in circuit where circuit elements meet
  - Wire between components are considered part of one node




What components?
How many nodes? 3

Where are these nodes?




#### **Breadboard**

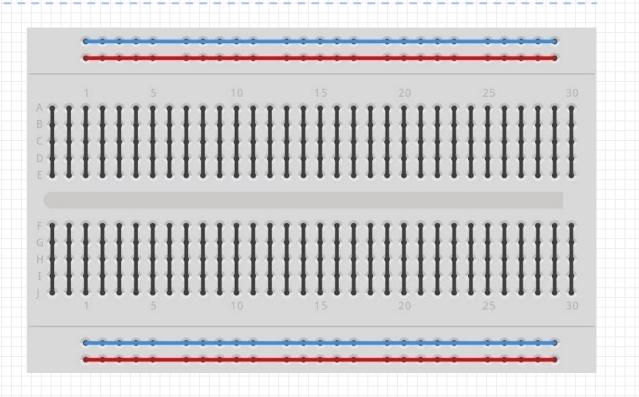




#### **Breadboard**

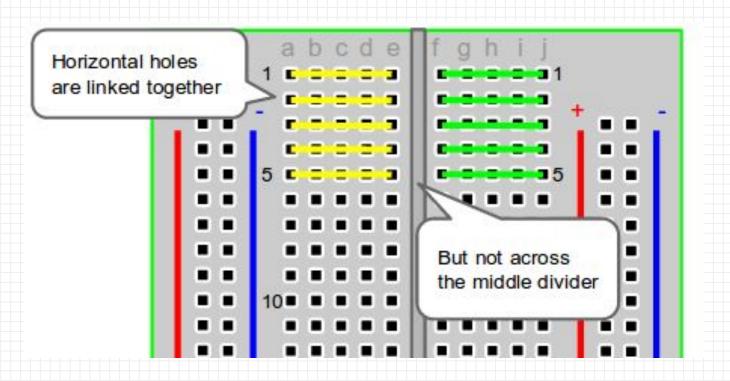



# Light-detecting Circuit

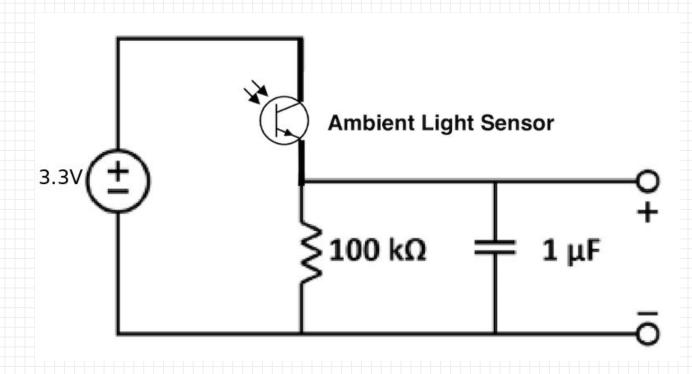






Please use the station desktops for this lab.

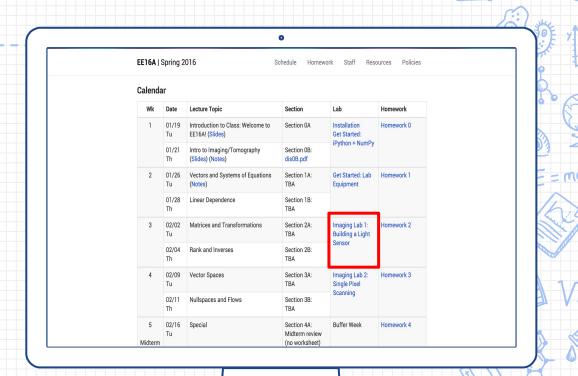This week's lab is listed as "Imaging Lab 1"



# FAQ

- ✗ UNZIP the downloaded file before doing anything ask us if you have questions
- ★ SHIFT+RIGHT CLICK on a folder window to open in CMD
  - X 'ipython notebook' to open ipython notebook
  - Let us know **IMMEDIATELY** if you're having trouble with this
- Never have the output of the voltage source on while you are moving things around
- × Probes are in the back
- ✗ Make sure you are using the right resistor (Brown Black Gold) get at TA desk
- **X** Make sure your Phototransistor is the right direction
- **X** DO NOT MESS WITH THE INSTALL DO NOT PIP INSTALL ANYTHING
- Complete the lab in **PAIRS**, do ONE setup per group