

# EE16A Lab: Touchscreen 2



- Building the base of the resistive touchscreen
- Resistors in parallel and in series
- Breadboarding!


- Investigate a resistive touchscreen
  - Something cool that actually was used for a long time!
- Use voltage as a signal to determine position of touch
  - How?

## Resistive Touchscreen


- Physical touch results in physical contact between top and bottom layers
- Voltage dividers allow us to compute touch location

EX: Nokia N900, Nokia N97 Mini, LG Optimus, LG GW620, Nintendo DS

TM

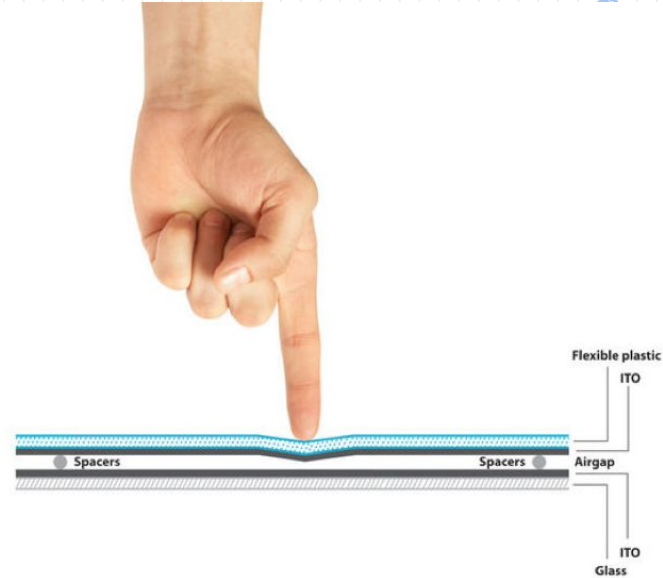

Resistive touchscreen

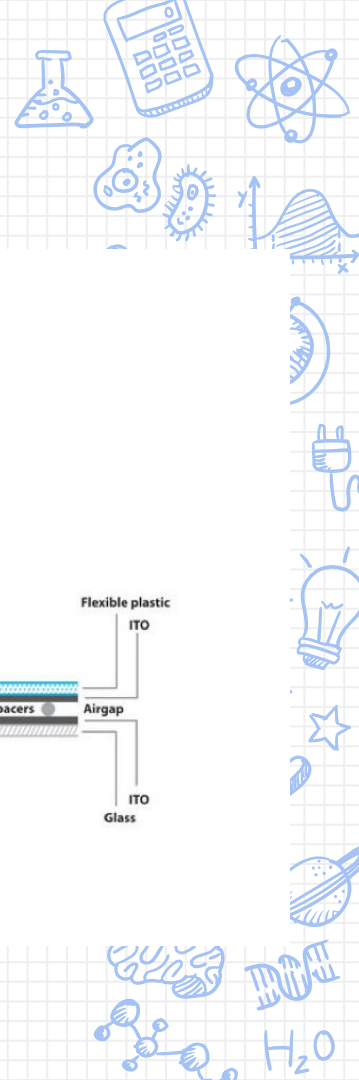

## Tools for Today:


---

- Power Supply
  - Always set a current limit! (0.1 A)
- Multimeter - measuring device
- Launchpad - measuring device
- Voltage dividers
  - How we will detect location


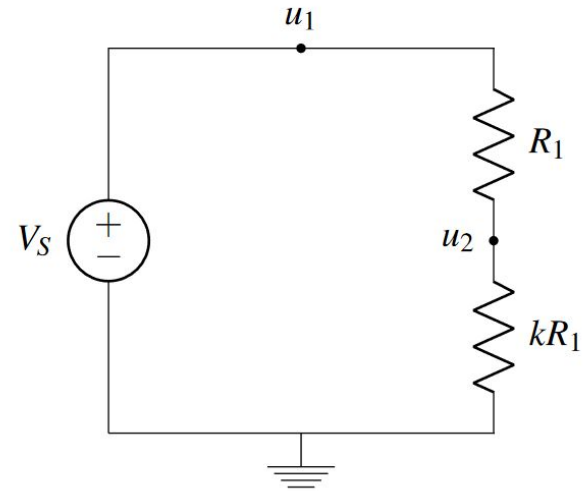
# Touchscreen Theory (Note 13/14)

- What's the voltage at the top?
- What's the voltage at the bottom?
- Voltage at  $u_2$ ?



# Touchscreen Theory (Note 13/14)


- Voltage divider:


$$u_2 = V_s * \frac{kR_1}{kR_1 + R_1}$$

$$u_2 = V_s * \frac{R_1(k)}{R_1(k+1)}$$

$$u_2 = V_s * \frac{k}{k+1}$$

Independent of  
the value of R!

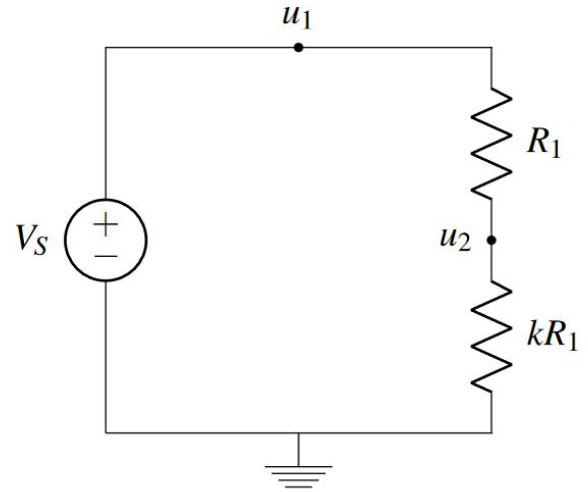

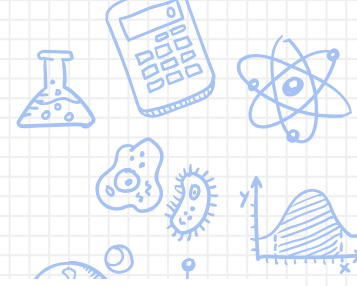


## Build it up

- What are the voltages at  $u_2$  and  $u_3$ ?

$$u_2 = V_s * \frac{k}{k+1}$$


$$u_3 = V_s * \frac{k}{k+1}$$

- What's the voltage difference?

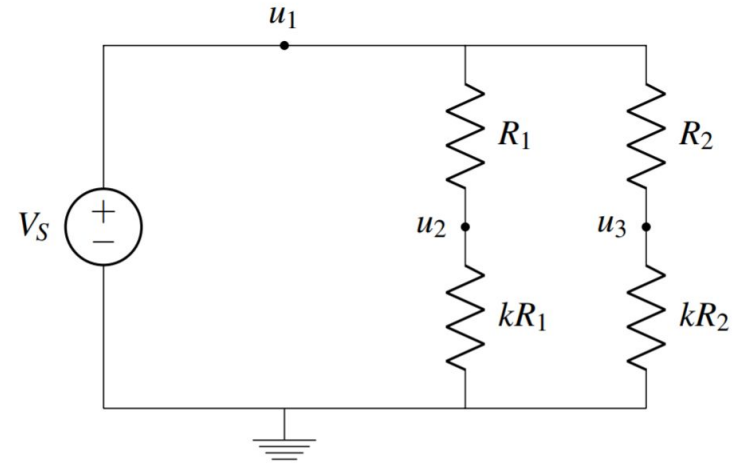

The  $R$ s cancel out! All that matters is the proportion between the top and bottom resistors.

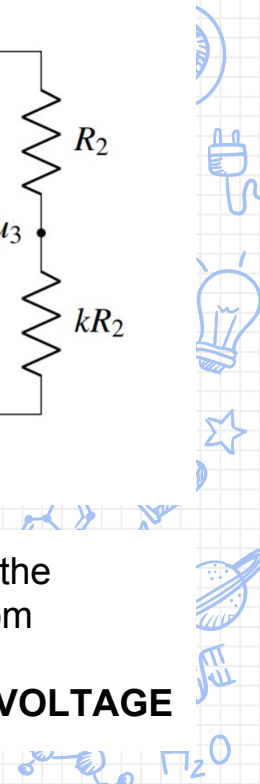In fact,  **$u_3$  and  $u_2$  are at the SAME VOLTAGE**







## Building it up

- We know that  $u_2 - u_3 = 0$
- **How much current goes through  $R_3$ ?**

$$u_2 = V_s * \frac{k}{k+1}$$


$$u_3 = V_s * \frac{k}{k+1}$$

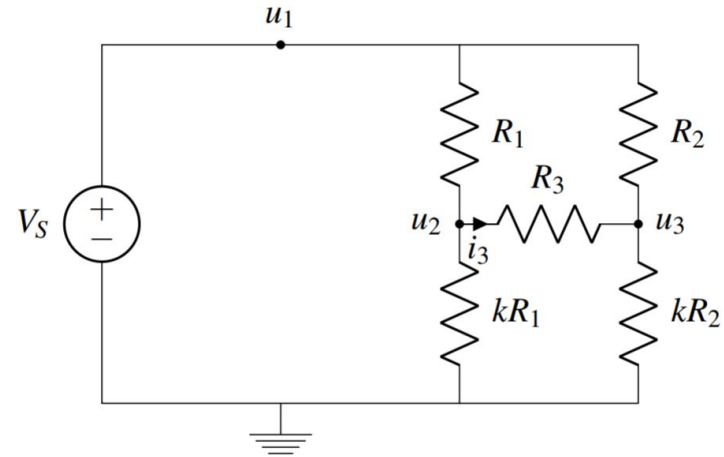

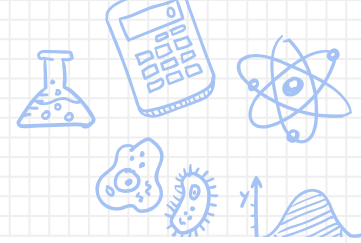



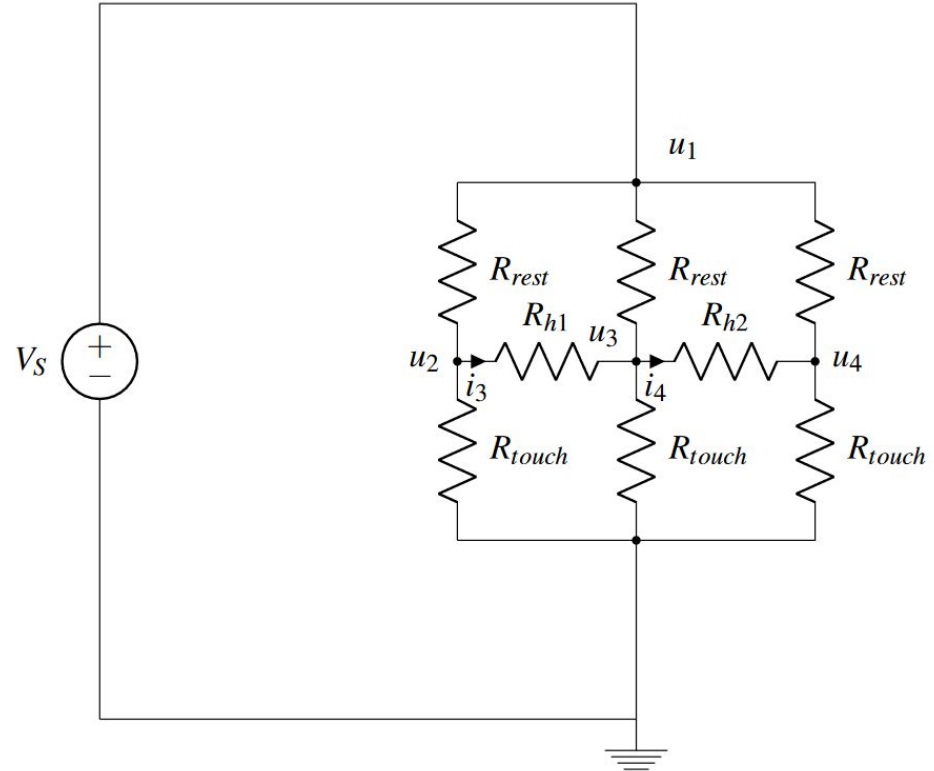
## Building it up

- Add one more resistor divider...
- We get our touchscreen!




# Resistive Touchscreen - 2 Layers

## Bottom Layer: Resistive Layer

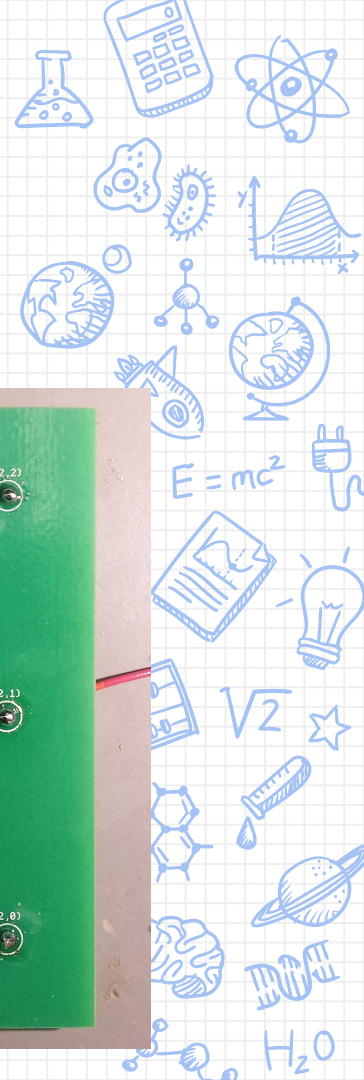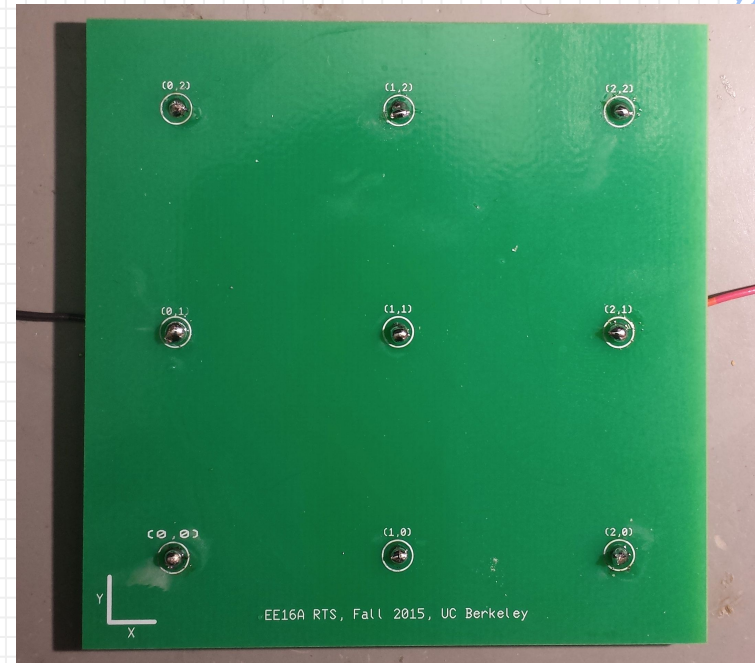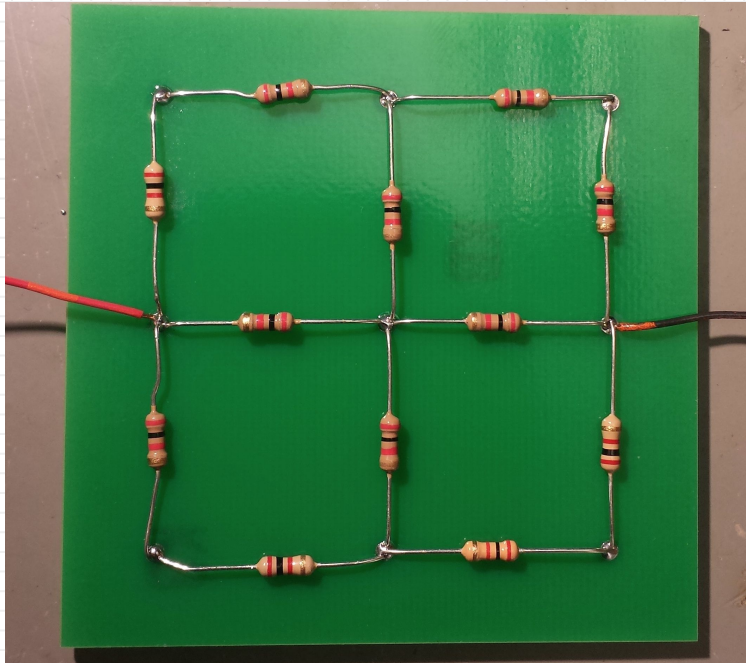

# Resistive Touchscreen - 2 Layers

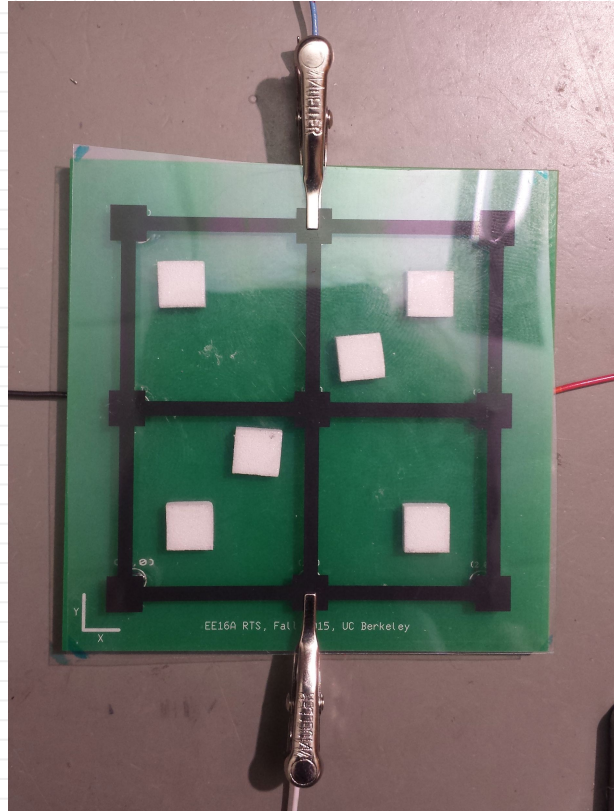

Top Layer:  
Flexible Resistive  
Layer



# What's The Difference?


---

- Nothing
  - The ink is just a bunch of resistors
    - The resistor values don't matter because we showed only the proportions matter for this circuit
  - Their circuit diagrams are the same
- One is just flexible so we can actually move it to make contact
- We use two so that we can measure with one and apply voltage to the other without changing our circuit. More on this in the next slides


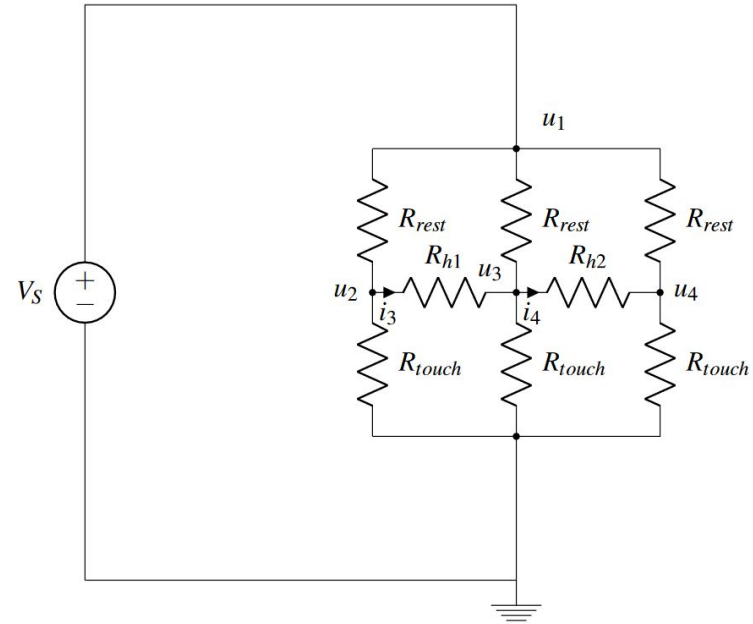
## Actually Computing a Location


- Measure some voltages, compute location based on value
- **What about horizontally?**
- **Can you find any two horizontal locations that would give the same voltage?**




## Actually Computing a Location

- We can only get a solution vertically
- What about the other dimension?


What if we  
turned it  
sideways?

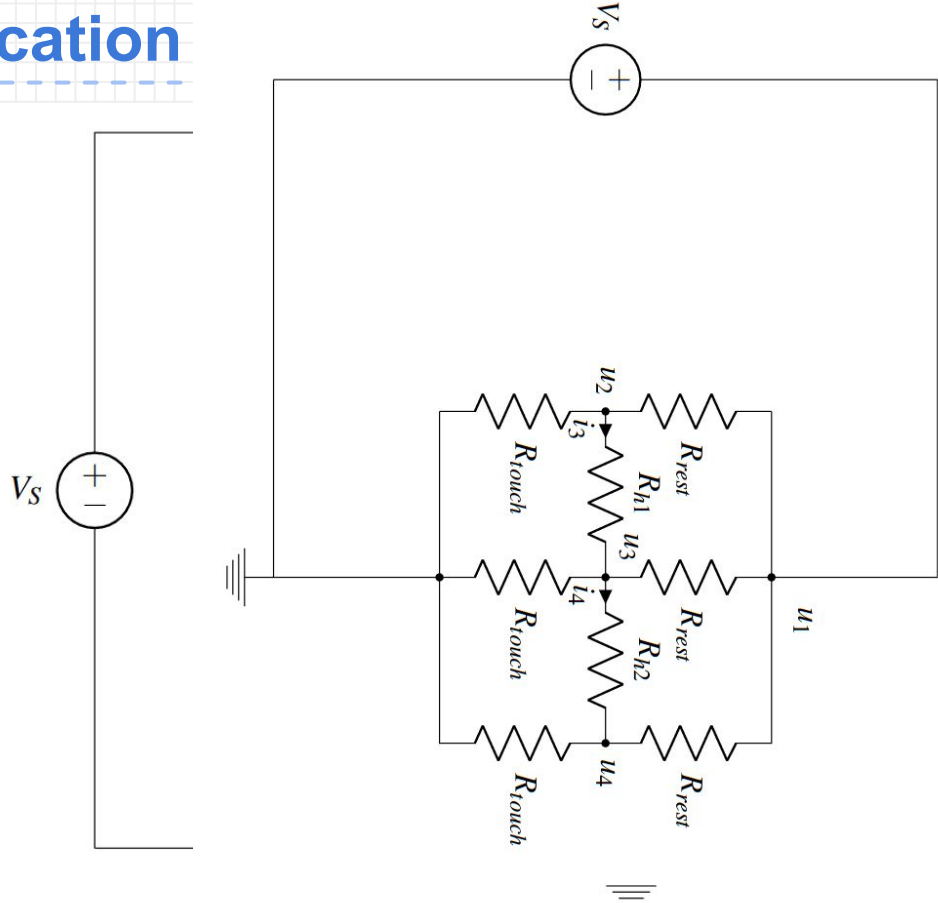

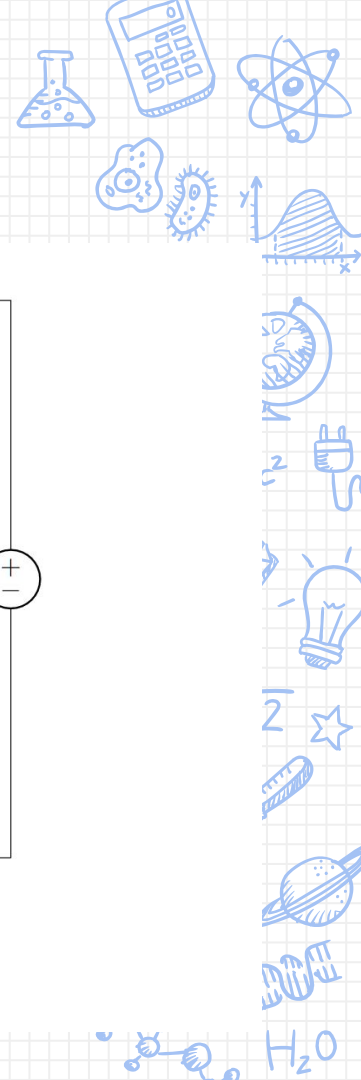
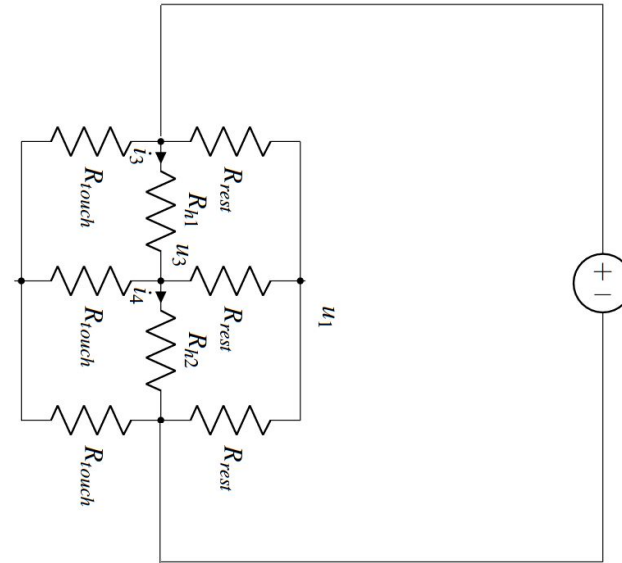
## Actually Computing a Location

- Let's turn it sideways
  - Apply voltage so we power the horizontal direction
  - Find “vertical” location in horizontal orientation
- This gives horizontal location





- If we take two readings, one in each dimension can uniquely determine our location in 2D
- More on this in the lab

# Taking the Limit

---

- 9 touch points is kinda meh
- **How do we get more?**



-

- But what if I don't want to increase the size of the circuit
  - Add more, but make the resistors smaller!
- What happens as the resistors approach infinitely small sizes?
  - Isn't that just a resistive sheet?
  - This is how all resistive touchscreens work

# Notes

---

- Make sure **ink side** of the plastic film is **facing down** towards the resistors
- There are coordinates on the PCB (**use them**)
- Foam blocks and film are on the TA desk
- Make sure you close serial monitor before running the ipython code
- Read **carefully** for which coordinates you should be connecting the multimeter and the power supply to
  - One wire will be free & 3 wires will be in use

