

---

# EECS 16A      Designing Information Devices and Systems I

## Fall 2018      Homework 7

---

**This homework is due October 12, 2018, at 23:59.**

**Self-grades are due October 16, 2018, at 23:59.**

### Submission Format


Your homework submission should consist of **one** file.

- `hw7.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

Submit the file to the appropriate assignment on Gradescope.
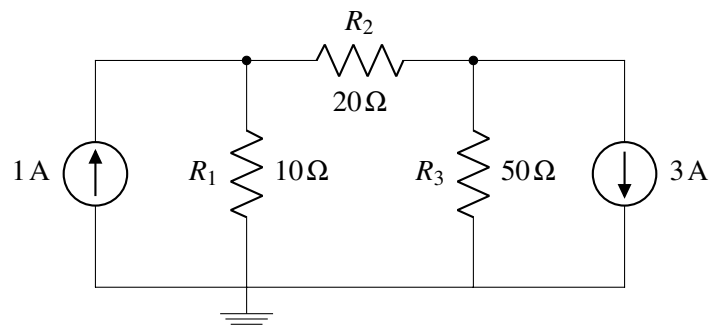
### 1. Circuit Analysis

Solve the circuit given below for all the currents and all the node voltages.



### 2. Cell Phone Battery

As great as smartphones are, one of their main drawbacks is that their batteries don't last a very long time. A Google Pixel, under somewhat regular usage conditions (internet, a few cat videos, etc.) uses 0.3 W of power. We will model the battery as a voltage source (which, as you know, will maintain a voltage across its terminals regardless of current through it) with one caveat: they have a limited amount of charge, or capacity. When the battery runs out of charge, it no longer provides a constant voltage, and your phone dies. Typically, engineers specify battery capacity in terms of mAh, which indicates how many mA of current the battery can supply for one hour before it needs to be recharged. The Pixel's battery has a battery capacity of 2770mAh and operates at a voltage of 3.8 V.

- When a battery's capacity is depleted, it no longer operates as a voltage source. How long will a Pixel's full battery last under regular usage conditions?
- How many coulombs of charge does the battery contain? Recall that  $1\text{ C} = 1\text{ A} \times 1\text{ s}$ , which implies that  $1\text{ mC} = 1\text{ mAs}$ . An electron has approximately  $1.602 \times 10^{-19}\text{ C}$  of charge. How many usable electrons worth of charge are contained in the battery when it is fully charged?
- Suppose the cell phone battery is completely discharged and you want to recharge it completely. How much energy (in J) is this? Recall that a J is equivalent to a W s.

- (d) Suppose PG&E charges \$0.12 per kWh. Every day, you completely discharge the battery (meaning more than typical usage) and you recharge it every night. How much will recharging cost you for the month of October (31 days)?
- (e) The battery has internal circuitry that prevents it from getting overcharged (and possibly exploding!). The circuitry is also used to transfer power into the chemical reactions that store the energy. We will model this internal circuitry as being one resistor with resistance  $R_{\text{bat}}$ , which is typically a small, non-negative resistance. Furthermore, we'll assume that all the energy dissipated across  $R_{\text{bat}}$  goes to recharging the battery. Suppose the wall plug and wire can be modeled as a 5 V voltage source and 200 m $\Omega$  resistor, as pictured in Figure 1. What is the power dissipated across  $R_{\text{bat}}$  for  $R_{\text{bat}} = 1 \text{ m}\Omega$ , 1  $\Omega$ , and 10 k $\Omega$ ? How long will the battery take to charge for each of those values of  $R_{\text{bat}}$ ?

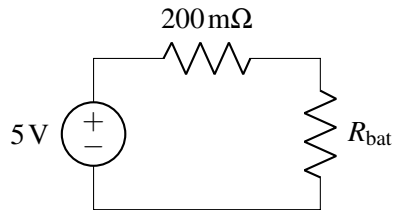



Figure 1: Model of wall plug, wire, and battery.

### 3. Fruity Fred

Fruity Fred just got back from Berkeley Bowl with a bunch of mangoes, pineapples, and coconuts. He wants to sort his mangoes in order of weight, so he decides to use his knowledge from EE16A to build a scale.

He finds two identical bars of material ( $M_1$  and  $M_2$ ) of length  $L$  (meters) and cross-sectional area  $A_c$  (meters<sup>2</sup>), which are made of a material with resistivity  $\rho$ . He knows that the length of these bars decreases by  $k$  meters per Newton of force applied, while the cross-sectional area remains constant.

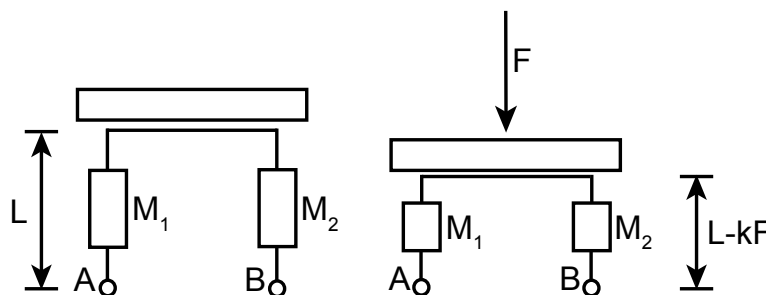He builds his scale as shown below, where the top of the bars are connected with an ideal electrical wire. The left side of the diagram shows the scale at rest (with no object placed on it), and the right side shows it when the applied force is  $F$  (Newtons), causing the length to decrease by  $kF$  meters. Fred's mangoes are not very heavy, so  $L \gg kF$ .



- (a) Let  $R_{AB}$  be the resistance between nodes A and B. Write an expression for  $R_{AB}$  as a function of  $A_c$ ,  $L$ ,  $\rho$ ,  $F$ , and  $k$ .

- (b) Fred's scale design is such that the resistance  $R_{AB}$  changes depending on how much weight is placed on it. However, he really wants to measure a voltage rather than a resistance.

Design a circuit for Fred that outputs a voltage that is some function of the weight. Your circuit should include  $R_{AB}$ , and you may use any number of voltage sources and resistors in your design. Be sure to label where the voltage should be measured in your circuit. Also provide an expression relating the output voltage of your circuit to the force applied on the scale.


#### 4. Temperature Sensor

Measuring quantities in the physical world is the job of sensors. This means somehow extracting that information from the world and then converting it into a form that can be observed and processed. Electrical circuits can be very useful for doing this.


For most materials, resistance increases with increasing temperature; that is, a resistor has higher resistance when it is hot than when it is cold. This is often an annoyance to circuit designers who want their circuits to work the same way at different temperatures, but this fact can also be useful. It allows us to convert temperature, a "physical" quantity, into resistance, an "electrical" quantity, to build an electronic thermometer.

In this problem, we are going to explore how effective a particular circuit made out of various types of resistors is at allowing us to measure temperature.

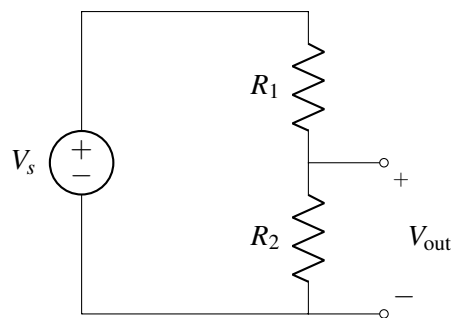
- (a) Let's begin by analyzing a common topology, the voltage divider shown below. Find an equation for the voltage  $V_{\text{out}}$  in terms of  $R_1$ ,  $R_2$ , and  $V_s$ .



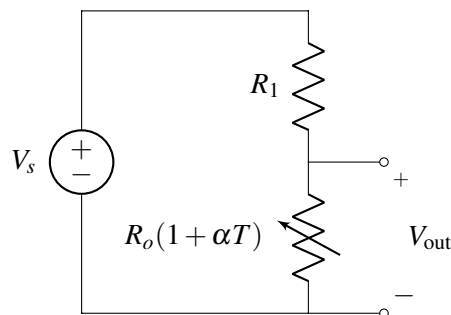
- (b) Now let's suppose that  $R_1$  is an ideal resistor that does not depend on temperature, but  $R_2$  is a temperature-dependent resistor whose resistance  $R$  is set by  $R = R_o(1 + \alpha T)$ , where  $T$  is the absolute temperature. Find an equation for the temperature  $T$  in terms of the voltage  $V_{\text{out}}$ ,  $V_s$ ,  $R_1$ ,  $R_o$ , and  $\alpha$ .



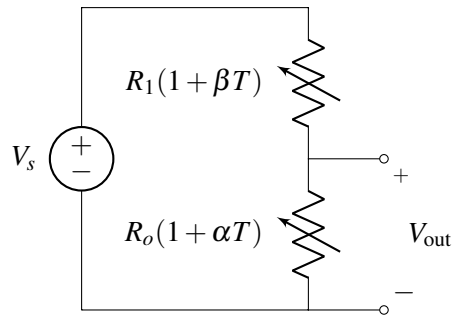- (c) It turns out that almost all resistors have some temperature dependence. Consider the same circuit as before, but now,  $R_1$  has a temperature dependence given by  $R'_1 = R_1(1 + \beta T)$ . Find an equation for the temperature  $T$  in terms of the voltage  $V_{\text{out}}$ ,  $R_1$ ,  $R_o$ ,  $V_s$ ,  $\alpha$ , and  $\beta$ .




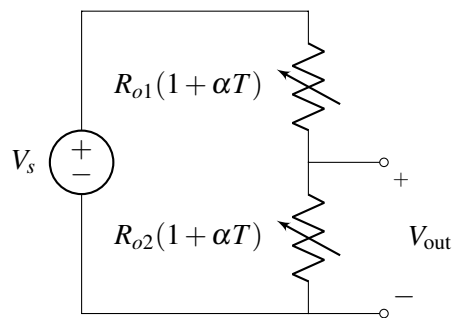- (d) Your colleague who has not taken EE16A thinks that they can improve this circuit's ability to measure temperature by making both resistors depend on temperature in the same way. He hence came up with the circuit shown below, where both  $R_1$  and  $R_2$  have nominally different values, but both vary with temperature as a function of  $(1 + \alpha T)$ . Can this circuit be used to measure temperature? Why or why not?



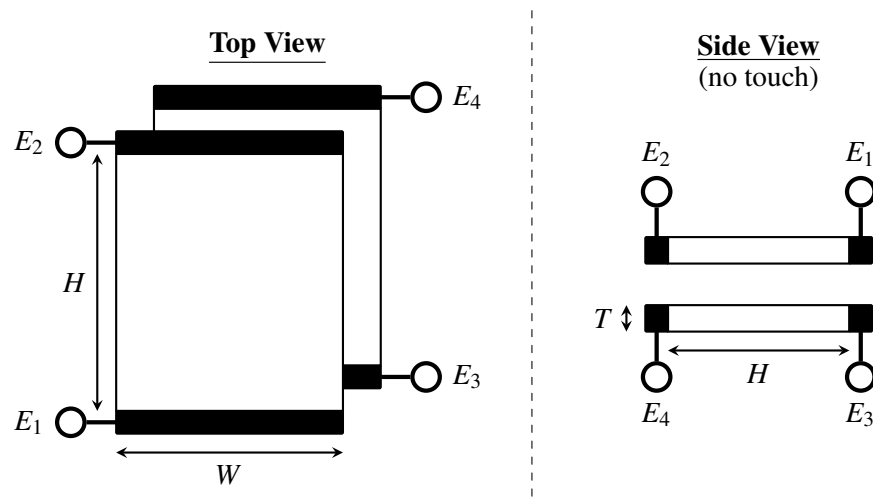
## 5. Multitouch Resistive Touchscreen


In this problem, we will look at a simplified version of the multitouch resistive touchscreen. In particular, rather than measuring the position of two potential touch points in both dimensions (i.e. a pair of coordinates  $(x_1, y_1)$  and  $(x_2, y_2)$  corresponding to two touch positions), let's think about a version where we are interested in measuring only the vertical position of the two touch points (i.e.  $y_1$  and  $y_2$ ). Therefore, unlike the touchscreens we looked at in class, both of the resistive plates (i.e. both the top and the bottom plate) would have conductive strips placed along their top and bottom edges, as shown below.



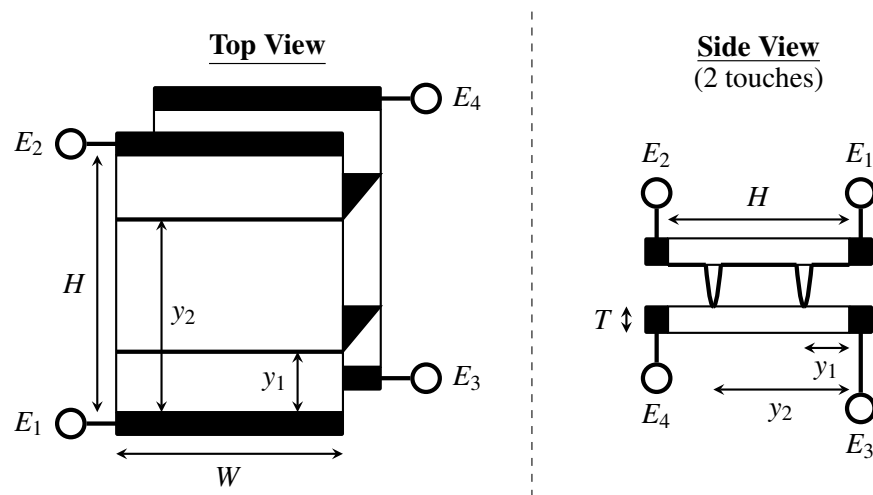- (a) Assuming that both of the plates are made out of a material with  $\rho = 1 \Omega\text{m}$  and that the dimensions of the plates are  $W = 3 \text{ cm}$ ,  $H = 12 \text{ cm}$ , and  $T = 1 \text{ mm}$ , with no touches at all, what is the resistance between terminals  $E_1$  and  $E_2$  (which would be the same as the resistance between terminals  $E_3$  and  $E_4$ )?
- (b) Now let's look at what happens when we have two touch points. Let's assume that at wherever height the touch occurs, a perfect contact is made between the top plate and the bottom plate along the entire width of the plates (i.e. you don't have to worry about any lateral resistors), but that otherwise none of the electrical characteristics of the plates change. Defining the bottom of the plate as being  $y = 0 \text{ cm}$  (i.e. a touch at  $E_1$  would be at  $y = 0 \text{ cm}$ ), let's assume that the two touches happen at  $y_1 = 3 \text{ cm}$  and  $y_2 = 7 \text{ cm}$  and that your answer to part (a) was  $8 \text{ k}\Omega$  (which may or may not be the right answer). Draw a model with 6 resistors that captures the electrical connections between  $E_1$ ,  $E_2$ ,  $E_3$ , and  $E_4$  and calculate their resistances. Note that for clarity, the system has been redrawn below to depict this scenario.



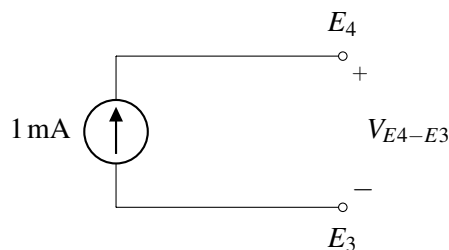- (c) Using the same assumptions as part (b), if you drove terminals  $E_3$  and  $E_4$  with a  $1 \text{ mA}$  current source (as shown below) but left terminals  $E_1$  and  $E_2$  open-circuited, what is the voltage you would measure across  $E_4 - E_3$  (i.e.  $V_{E4-E3}$ )?



- (d) Now let's try to generalize the situation by assuming that the two touches can happen at any two arbitrary points  $y_1$  and  $y_2$ , but with  $y_1$  defined to always be less than  $y_2$  (i.e.  $y_1$  is always the bottom touch point). Leaving the setup the same as in part (c) except for the arbitrary  $y_1$  and  $y_2$ , by measuring only the voltage between  $E_4$  and  $E_3$ , what information can you extract about the two touch positions? Please be sure to provide an equation relating  $V_{E4-E3}$  to  $y_1$  and  $y_2$  as a part of your answer, and note that you may want to redraw the model from part (b) to help you with this.
- (e) One of your colleagues claims that by measuring the appropriate voltages, not only can they extract what both  $y_1$  and  $y_2$  are in this system, but they can even do so by formulating a system of three

independent voltage equations related to  $y_1$  and  $y_2$ . As we will see later, this will allow us to gain some robustness to noise in the voltage measurements.

In order to facilitate this, write equations relating  $V_{E4-E2}$  and  $V_{E1-E3}$  to  $y_1$  and  $y_2$ . (The third voltage we'll use is  $V_{E4-E3}$ , which you should have already derived an equation for in the previous part of the problem.)

## 6. Homework Process and Study Group

Who else did you work with on this homework? List names and student ID's. (In case of homework party, you can also just describe the group.) How did you work on this homework?